

Parity generator and checker

A parity checker is used to detect errors during transmission of binary data. Parity bit is used to check the data.

Parity Generator :- The digital circuit that generates a parity bit in the transmitter is known as parity generator.

Parity Checker :- The digital circuit that checks the parity bit at the receiver is parity checker.

PARITY GENERATOR :-

Let's take an example of 7 bits


Even Parity



Data Bits
(1 One)

Parity bit → it will be 1

in the code.

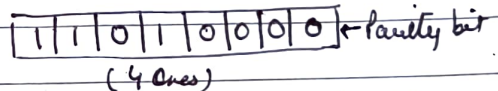

(4 Ones)

The no of 1's is even after adding the parity bit


Odd Parity



Data Bits
(4 Ones)

Parity Bits
(1)

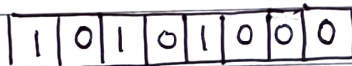The no of 1's in the code is odd after adding the parity bit



Data Bits
(3 Ones)

Parity Bit

Truth Table for 3 bit even parity generator


Input			Output
A	B	C	P _{even}
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$$P = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$

$$= \bar{A}(\bar{B}C + B\bar{C}) + A(\bar{B}\bar{C} + BC)$$

$$= \bar{A}(B \oplus C) + A(\overline{B \oplus C})$$

$$= A \oplus B \oplus C$$

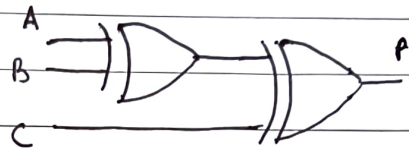

Truth Table of 3 bit ^{Odd} ~~even~~ parity generator

A	B	C	P _o
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	1	0	0
1	0	1	1
1	1	0	1
1	1	1	0

this truth table is complement of even parity generator. so we need to add a not gate at the end of the even parity generator

Parity Checker

- The parity checker circuit is at the receiver end.
- The output of the parity checker circuit is denoted by PEO Parity Error Output

PEO = 1 when the error is present i.e. if the received four bit word has even parity

PEO = 0 when there is no error present i.e. if the received four bit word has an odd parity

Even Parity Checker

A	B	C	P_{odd}	Parity Check	
0	0	0	0	0	
0	0	0	1	1	
0	0	1	0	1	
0	0	1	1	0	
0	1	0	0	1	$= \bar{A}\bar{B}\bar{C}P_0 + \bar{A}\bar{B}C\bar{P}_0$
0	1	0	1	0	$\bar{A}\bar{B}\bar{C}\bar{P}_0 + \bar{A}\bar{B}CP_0$
0	1	1	0	0	$A\bar{B}\bar{C}\bar{P}_0 + A\bar{B}C\bar{P}_0$
0	1	1	1	1	$\bar{A}B\bar{C}P_0 + \bar{A}BCP_0$
1	0	0	0	1	
1	0	0	1	0	$= \bar{A}\bar{B}(\bar{C}P_0 + C\bar{P}_0)$
1	0	1	0	0	$+ \bar{A}\bar{B}(\bar{C}\bar{P}_0 + CP_0)$
1	0	1	1	1	$+ A\bar{B}(\bar{C}\bar{P}_0 + CP_0)$
1	1	0	0	0	$+ AB(\bar{C}P_0 + C\bar{P}_0)$
1	1	0	1	1	$= \bar{A}\bar{B}(\bar{C}P_0 + C\bar{P}_0) + \bar{A}\bar{B}(\bar{C}\bar{P}_0 + CP_0)$
1	1	1	0	1	$+ A\bar{B}(\bar{C}\bar{P}_0 + CP_0) + A\bar{B}(\bar{C}P_0 + C\bar{P}_0)$
1	1	1	1	0	$= \bar{A}\bar{B} \oplus (\bar{C}P_0 + C\bar{P}_0)$
					$= A \oplus B \oplus C \oplus P$

This can be developed using kmap

This is the complement of the even parity checker


Odd parity checker

A	B	C	P
0	0	0	0
0	0		1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1

P odd checker



1
0
0
1
0
1
1
0
0
1
0
1
0
0
0
1
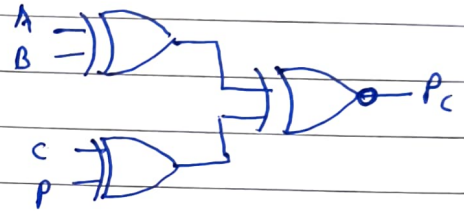
$$P_c = \overline{A \oplus B \oplus C + P}$$



IC: 74180 can be used as parity generator and parity checker


BCD TO 7 SEGMENT DECODER.

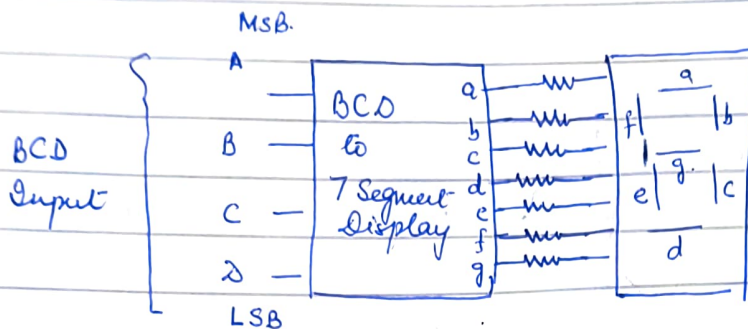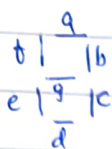

Decimal. Eg.	Decimal A B C D	a	b	c	d	e	f	g
0	0 0 0 0	1	1	1	1	1	1	0
1	0 0 0 1	0	1	1	0	0	0	0
2	0 0 1 0	1	1	0	0	0	0	1
3	0 0 1 1	1	1	1	1	0	0	1
4	0 1 0 0	0	1	1	0	0	1	1
5	0 1 0 1	1	0	1	1	0	1	1
6	0 1 1 0	1	0	1	0	1	1	1
7	0 1 1 1	1	1	1	0	0	0	0
8	1 0 0 0	1	1	1	1	1	1	1
9	1 0 0 1	1	1	1	0	0	0	1

↓ 9
10
15 Don't Care.

Make K-map for a

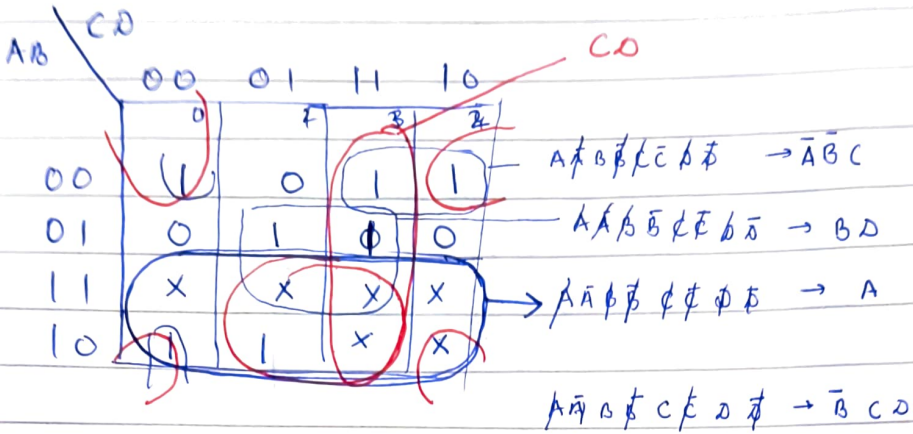

$$A + BD + \bar{A}\bar{B}C + \bar{B}CD + \bar{A}\bar{B}C$$

$$a = A + CD + \bar{B}\bar{D} + BD$$

